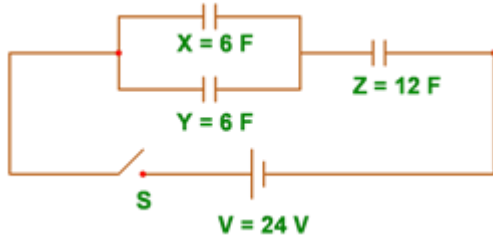


Directions: Solve for each of the below questions.

Problem 1

Given a circuit contains a combination of three capacitors X, Y and Z , see the figure below.



If the switch S is ON, find:

- a) circuit equivalent capacitance (equivalent capacitor)
- b) electric charge stored in the circuit
- c) electric charge stored in capacitor Z, use series principle
- d) potential difference across capacitor Z
- e) potential difference across capacitor X
- f) potential difference across capacitor Y
- g) electric charge stored in capacitor X
- h) electric charge stored in capacitor Y
- i) electric charge stored in capacitor Z
- j) energy stored in the circuit
- k) energy stored in capacitor X
- l) energy stored in capacitor Y
- m) energy stored in capacitor Z

Problem 2

Given a parallel-plate capacitor in vacuum. The plates of capacitor are 2 cm apart and 50 cm^2 in area of each plate. A potential difference of 120 volt is applied across capacitor. When ϵ_0 is $8,85 \times 10^{-12} \text{ C}^2 \text{ N}^{-1} \text{ m}^{-2}$ calculate :

a) capacitor capacitance

b) charge stored in capacitor

c) the magnitude of electric charge in space between the two plates of capacitor

Problem 3

A plate-capacitor of capacitance C in vacuum. If then a material with its dielectric constant $K = 2$ is inserted between capacitor plates, find the new capacitance of capacitor!

Problem 4

Given a parallel plate-capacitor of $1200 \mu\text{F}$ in vacuum. If the area of capacitor plates are doubled and the separation between two plates is 1.5 times the original, find the new capacitance of the capacitor!

Answer Key:

Problem 1 : Discussion

a) First replace X and Y parallel combination by its equivalent capacitance, named C_{xy} :

$$C_{xy} = C_x + C_y$$
$$C_{xy} = 6 + 6 = 12 \text{ F}$$

Replacing the two capacitors gives us the equivalent circuit in series combination, then find the equivalent for C_{xy} and C_z , the two are in series, called C_{eq} or C_{tot} :

$$\frac{1}{C_{tot}} = \frac{1}{C_{xy}} + \frac{1}{C_z}$$
$$\frac{1}{C_{tot}} = \frac{1}{12} + \frac{1}{12} = \frac{2}{12}$$
$$C_{tot} = \frac{12}{2} = 6 \text{ F}$$

b) Charge stored in the circuit or the charge in the equivalent capacitance; Q_{tot} , C_{tot} multiplied by V_{tot}

$$Q_{tot} = C_{tot} V_{tot} = 6(24) = 144 \text{ C}$$

c) Charge stored in capacitor Z; Q_z

For series combination, the charge is the same on all capacitors, it's the same as the charge on the equivalent capacitor :

$$Q_{xy} = Q_z = Q_{tot}$$
$$Q_z = 144 \text{ C}$$

d) potential difference across capacitor Z; named V_z

$$V_z = \frac{Q_z}{C_z} = \frac{144}{12} = 12 \text{ Volt}$$

e) potential difference across capacitors X and Z are the same cause of parallel combination

$$V_x = V_{xy} = \frac{Q_{xy}}{C_{xy}} = \frac{144}{12} = 12 \text{ Volt}$$

f) potential difference across Y is the same as potential difference across X

$$V_y = V_x = 12 \text{ Volt}$$

g) charge in capacitor X, be careful, it's not the same as charge in equivalent capacitor

$$Q_x = C_x V_x = 6(12) = 72 \text{ C}$$

h) charge in capacitor Y

$$Q_y = C_y V_y = 6(12) = 72 \text{ C}$$

i) charge in capacitor Z

$$Q_z = C_z V_z = 12(12) = 144 \text{ C}$$

j) energy stored in the circuit

Use one of these three formula to get the energy stored

$$W = \frac{1}{2} C V^2$$

$$W = \frac{1}{2} \frac{Q^2}{C}$$

$$W = \frac{1}{2} Q V$$

So then

$$W_{tot} = \frac{1}{2} C_{tot} V_{tot}^2 = \frac{1}{2} (6)(24)^2 = 1728 \text{ joule}$$

k) energy stored in capacitor X

$$W_x = \frac{1}{2} C_x V_x^2 = \frac{1}{2} (6)(12)^2 = 432 \text{ joule}$$

l) energy stored in capacitor Y

$$W_y = \frac{1}{2} C_y V_y^2 = \frac{1}{2} (6)(12)^2 = 432 \text{ joule}$$

m) energy stored in capacitor Z

$$W_z = \frac{1}{2} C_z V_z^2 = \frac{1}{2} (12)(12)^2 = 864 \text{ joule}$$

Problem 2: Answer

a) capacitor capacitance

$$C = \frac{kA\epsilon_o}{d}$$
$$C = \frac{(1)(50 \times 10^{-4})(8,85 \times 10^{-12})}{2 \times 10^{-2}} = 2,2 \times 10^{-12} = 2,2 \text{ pF}$$

b) charge stored in capacitor

$$Q = CV$$
$$Q = (2,2 \times 10^{-12})(120) = 264 \times 10^{-12} = 264 \text{ pC}$$

c) the magnitude of electric charge in space between the two plates of capacitor

$$E = \frac{V}{d}$$
$$E = \frac{120}{2 \times 10^{-2}} = 6000 \text{ V/m}$$

Problem 3: Answer

There are no changing in area and plates separation distance of capacitor, so then the new capacitance is

$$\frac{C_2}{C_1} = \frac{k_2}{k_1}$$
$$\frac{C_2}{C} = \frac{2}{1}$$
$$C_2 = 2C$$

Problem 4: Answer

$$C = \frac{kA\epsilon_o}{d}$$
$$\frac{C_2}{C_1} = \frac{A_2}{A_1} \times \frac{d_1}{d_2}$$
$$\frac{C_2}{1200} = \frac{(2)(1)}{(1)(1,5)}$$
$$C_2 = \frac{2}{1,5} \times 1200 = 1600 \text{ } \mu\text{F}$$