

Show all of your work! Label all units!

1. A battery is connected in series with a variable resistor and an ammeter. When the resistance of the resistor is $10\ \Omega$ the current is $2.0\ \text{A}$. When the resistance is $5\ \Omega$ the current is $3.8\ \text{A}$. Find the emf and the internal resistance of the battery. 10 pts.

2. A copper wire has a cross-sectional area of $5.0 \times 10^{-7}\ \text{m}^2$ and a length of $10.0\ \text{m}$. An aluminum wire of exactly the same dimensions is welded to the end of the copper wire. The ends of this long copper-aluminum wire are connected to a 3.0-volt battery. Neglect the resistance of any other wires in the figure.

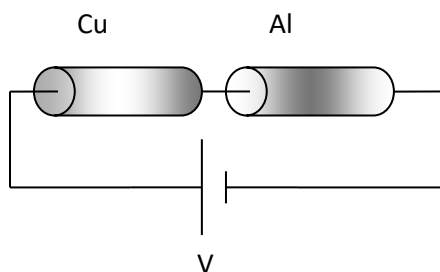



Figure not drawn to scale

Determine

- (a) the total resistance of the circuit. 3 pts.
- (b) the total current in the wire. 2 pts.

3. Which of the following wires is likely to have the greatest resistance? 5 pts.
- A copper wire 0.2 mm thick and 10 cm long
 - A Nichrome wire 0.2 mm thick and 10 cm long
 - A Nichrome wire 0.1 mm thick and 15 cm long
 - A copper wire 0.3 mm thick and 5 cm long.

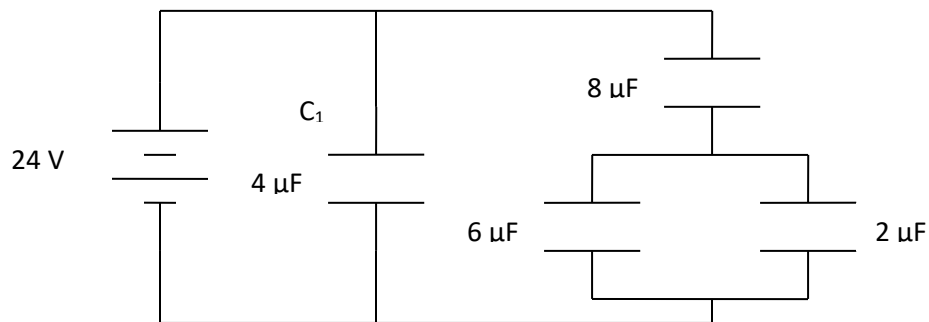
4. In the diagram below, determine the value in each of the below parts of the problem



- Find the equivalent capacitance of the capacitors above. 4 pts
- Determine the total charge in the circuit. 2 pts.
- Determine the charge on one plate of C_1 . 2 pts.
- Determine the electrical energy stored in C_1 . 2 pts.

5. A light bulb oven is left on for 3 hrs and consumes 18 Watt hours of electricity. If the bulb draws a current of 0.3A, what is the resistance of the bulb? 5 pts.

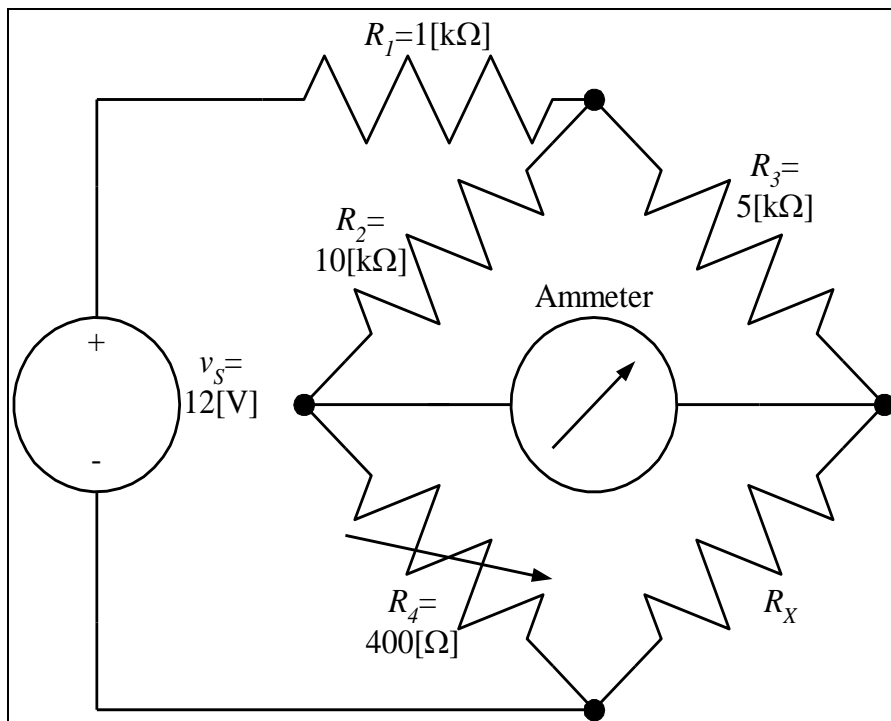6. The ammeter shown has a meter resistance of $100[\Omega]$. Resistor R_4 has been adjusted so that the ammeter will read zero. Find the value of R_x for this situation. 5 pts.



7. RC circuit: Show all of your work and label all units. 10 pts.

*Analyze the circuit below to find the charge stored on each capacitor at steady state.

