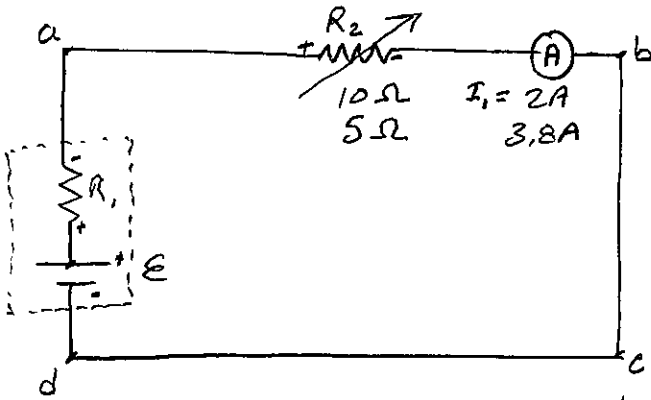


Show all of your work! Label all units!

1. A battery is connected in series with a variable resistor and an ammeter. When the resistance of the resistor is $10\ \Omega$ the current is $2.0\ \text{A}$. When the resistance is $5\ \Omega$ the current is $3.8\ \text{A}$. Find the emf and the internal resistance of the battery. 10 pts.



USE KIRCHHOFF RULES KVL.
a b c d: $-I_1 R_2 + E - I_1 R_1 = 0$
 $E = I_1 R_1 + I_1 R_2$
 $E = 2 R_1 + 2(10)$

- now with new (different) resistor
a b c d: $-I_2 R_2 + E - I_2 R_1 = 0$

$$E = I_2 R_1 + I_2 R_2$$

$$E = 3.8 R_1 + 3.8(5)$$

Since: $E_1 = E_2$

$$2 R_1 + 20 = 3.8 R_1 + 19$$

$$1 = 1.8 R_1$$

$$0.556\ \Omega = R_1$$

Now substitute R_1 into either equation

$$E_1 = 2(0.556) + 20$$

$$E_1 = 21.11\ \text{V}$$

2. A copper wire has a cross-sectional area of $5.0 \times 10^{-7}\ \text{m}^2$ and a length of $10.0\ \text{m}$. An aluminum wire of exactly the same dimensions is welded to the end of the copper wire. The ends of this long copper-aluminum wire are connected to a 3.0-volt battery. Neglect the resistance of any other wires in the figure.

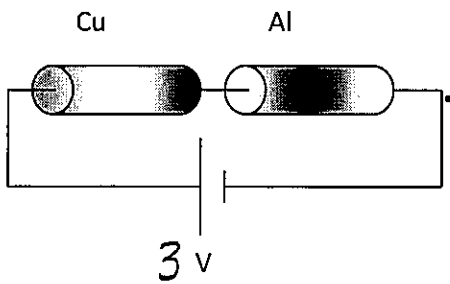


Figure not drawn to scale

$$a) R_{Cu} = \rho \frac{L}{A} = 1.72 \times 10^{-8}\ \Omega \cdot \text{m} \times \frac{10\ \text{m}}{5 \times 10^{-7}\ \text{m}^2}$$

$$R_{Cu} = 0.344\ \Omega$$

$$R_{Al} = \rho \frac{L}{A} = 2.83 \times 10^{-8}\ \Omega \cdot \text{m} \times \frac{10\ \text{m}}{5 \times 10^{-7}\ \text{m}^2}$$

$$R_{Al} = 0.566\ \Omega$$

Determine

- (a) the total resistance of the circuit. 3 pts.
(b) the total current in the wire. 2 pts.

Since in Series = $R_{Cu} + R_{Al} = 0.9\ \Omega$

$$b) I = \frac{V}{R} = \frac{3\ \text{V}}{0.9\ \Omega} = 3.33\ \text{A}$$

3. Which of the following wires is likely to have the greatest resistance? 2pts.

- A copper wire 0.2 mm thick and 10 cm long
- A Nichrome wire 0.2 mm thick and 10 cm long
- A Nichrome wire 0.1 mm thick and 15 cm long
- A copper wire 0.3 mm thick and 5 cm long.

$$R = \rho \frac{L}{A(\pi r^2)}$$


$$a) R = \rho \frac{L}{A} = 1.72 \times 10^{-8} \Omega \cdot m \times \frac{0.1 m}{3.14 \cdot (0.0001 m)^2} = \frac{1.72 \times 10^{-9} \Omega \cdot m^2}{3.14 \times 10^{-8} m^2} = 0.0548 \Omega$$

$$b) R = \rho \frac{L}{A} = 110 \times 10^{-8} \Omega \cdot m \times \frac{0.1 m}{3.14 \cdot (0.0001 m)^2} = \frac{1.1 \times 10^{-7} \Omega \cdot m^2}{3.14 \times 10^{-8} m^2} = 3.5 \Omega$$


$$c) R = \rho \frac{L}{A} = 110 \times 10^{-8} \Omega \cdot m \times \frac{0.15 m}{3.14 \cdot (0.00005 m)^2} = \frac{1.65 \times 10^{-7} \Omega \cdot m^2}{7.85 \times 10^{-9} m^2} = \boxed{21.02 \Omega}$$

$$d) R = \rho \frac{L}{A} = 1.72 \times 10^{-8} \Omega \cdot m \times \frac{0.05 m}{3.14 \cdot (0.15)^2} = \frac{8.6 \times 10^{-10} \Omega \cdot m^2}{7.065 \times 10^{-2} m^2} = 1.22 \times 10^{-8} \Omega$$

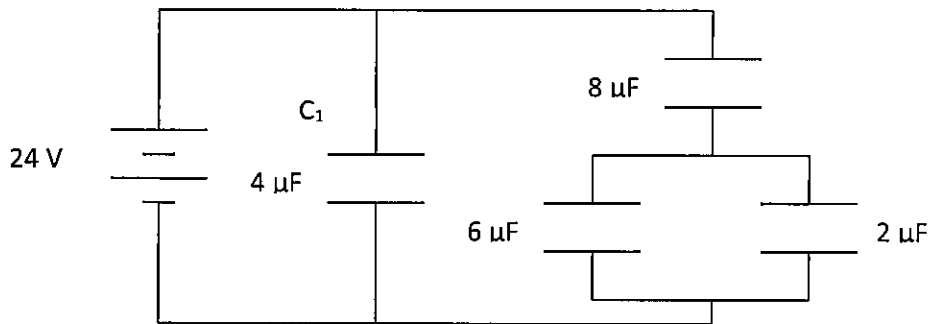4. In the diagram below, determine the value in each of the below parts of the problem



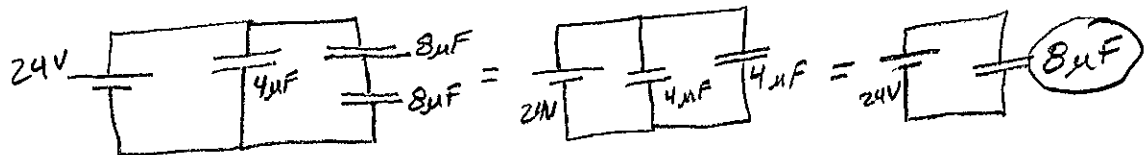a. Find the equivalent capacitance of the capacitors above. 4 pts



b. Determine the total charge in the circuit. 2 pts.

$$Q_T = CV = 8 \mu F \cdot 24 V = \boxed{192 \mu C}$$

c. Determine the charge on one plate of C_1 . 2 pts.

C_1 is in parallel with the battery so has 24 volts

$$Q_1 = C_1 V = 4 \mu F \cdot 24 V = 4 \frac{\mu C}{V} \cdot 24 \frac{V}{1} = \boxed{96 \mu C}$$

d. Determine the electrical energy stored in C_1 . 2 pts.

$$u = \frac{1}{2} \frac{Q^2}{C}$$

$$u = \frac{1}{2} QV$$

$$u = \frac{1}{2} CV^2 = \frac{1}{2} 4 \mu \frac{C^2}{V} \times (24 \frac{V}{1})^2 = \boxed{1152 \mu J}$$

5. A light bulb oven is left on for 3 hrs and consumes 18 Watt hours of electricity. If the bulb draws a current of 0.3A, what is the resistance of the bulb? 3 pts.

$$P = V \cdot I$$

$$P = I^2 R$$

$$E = P \cdot t$$

$$E = I^2 R \cdot t$$

$$E = 18 \text{ W} \cdot 3 \text{ hr} \Rightarrow 54 \text{ Wh} \cdot \frac{1}{1000} = 0.054 \text{ kWh}$$

$$0.054 \text{ kWh} = (0.3 \text{ A})^2 R \cdot 3 \text{ hr} \cdot 3600 \text{ s/hr}$$

$$0.018 \text{ kW} = 0.09 \text{ A}^2 \cdot R$$


$$18 \text{ W} = 0.09 \text{ A}^2 \cdot R$$

$$\frac{18 \text{ J/s}}{0.09 \text{ A}^2} = R$$

$$R = 200 \frac{\text{J/s}}{\text{A}^2} \text{ or } 200 \Omega$$

6. The ammeter shown has a meter resistance of $100[\Omega]$. Resistor R_4 has been adjusted so that the ammeter will read zero. Find the value of R_X for this situation. 5 pts.

BALANCED WHEATSTONE BRIDGE!

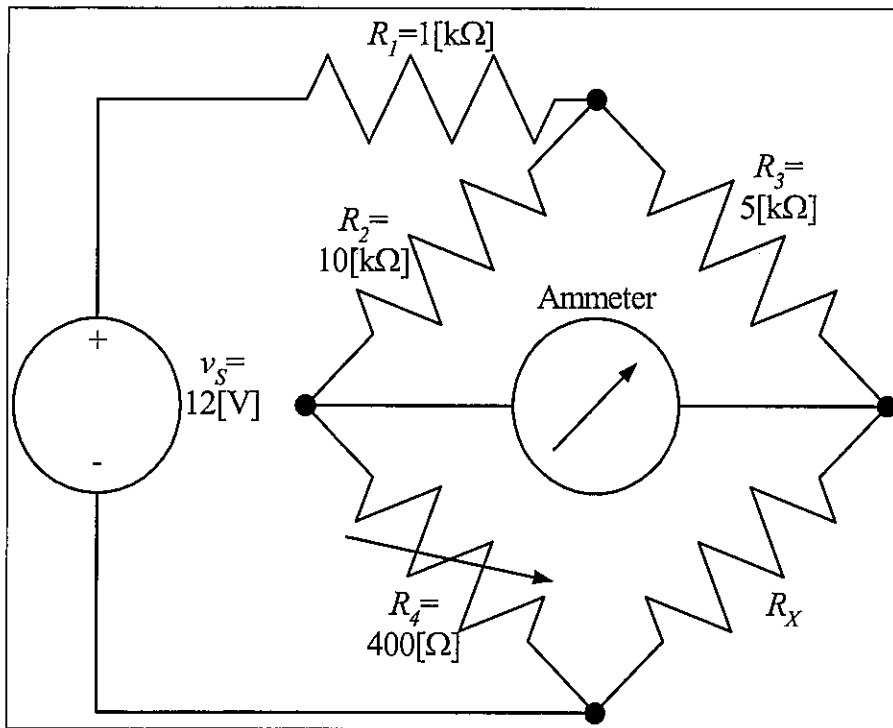

$$\frac{R_3}{R_2} = \frac{R_X}{R_4}$$


$$R_2 \cdot R_X = R_3 \cdot R_4$$

$$R_X = \frac{R_3 \cdot R_4}{R_2} = \frac{5000 \Omega \cdot 400 \Omega}{10,000 \Omega}$$

$$R_X = 200 \Omega$$

Bonus: RC circuit: Show all of your work and label all units. 4 pts.

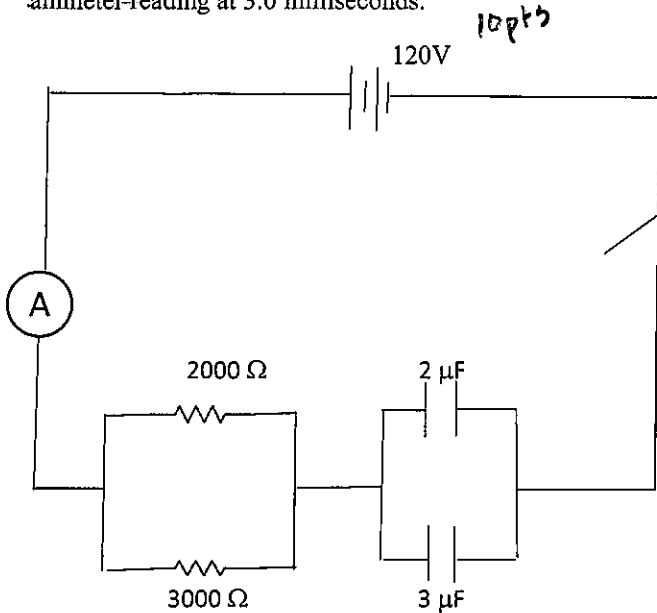*Analyze the circuit below to find the charge stored on each capacitor at steady state. Additionally, find the ammeter-reading at 3.0 milliseconds. 10 pts.



$$2 \mu\text{F}: Q = CV = 2 \times 10^{-6} \text{ F} \cdot 120 \text{ V}$$


$$Q = 2.4 \times 10^{-4} \text{ C}$$

$$3 \mu\text{F}: Q = CV = 3 \times 10^{-6} \text{ F} \cdot 120 \text{ V}$$

$$Q = 3.6 \times 10^{-4} \text{ C}$$

AT "STEADY STATE" THE CAPACITORS ARE FULL, THUS CURRENT STOPS FLOWING. THE VOLTAGE IN THE ABOVE DIAGRAM GIVES 120V TO EACH CAPACITOR, BECAUSE THEY ARE IN PARALLEL TO 2 μF & 3 μF CAPACITOR GET THE SAME VOLTAGE (120V). THE RESISTORS AT "STEADY STATE" DON'T HAVE CURRENT FLOWING, SO NO VOLTAGE DIFFERENCE.

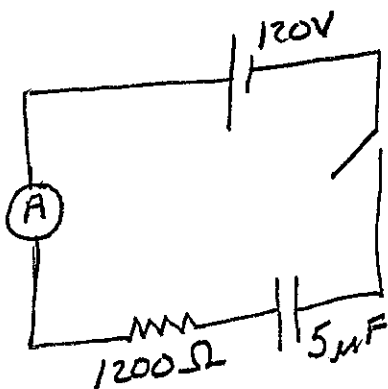TO FIND CURRENT AT $t = 3 \text{ ms}$ WE NEED TO KNOW MAX CURRENT AND TIME CONSTANT. THE EQUIVALENT RESISTANCE IS 1200Ω & CAPACITANCE IS $5 \mu\text{F}$.



$$I_{\text{max}} = \frac{V}{R} = \frac{120 \text{ V}}{1200 \Omega} = 0.1 \text{ A}$$

$$T = RC = 1200 \Omega \cdot 5 \times 10^{-6} \text{ F} = 0.006 \text{ sec}$$

$$I = I_{\text{max}} e^{-t/RC} = 0.1 (e^{-0.003/0.006}) = 0.061 \text{ A}$$